

## MOCK TEST PAPER # 2


### SOLUTION

#### IITJEE (Main) PHYSICS

1.(1) The equivalent circuit is:

Rest of the resistors are shorted.

$$\therefore R_{AB} = 2R$$

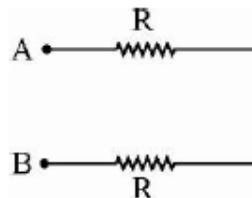

2.(4) For maximum current, net resistance of cells must be equal to  $2.5\Omega$

$$\text{i.e., } \frac{n(0.5)}{m} = 2.5 \quad \dots(1)$$

$$\text{and } m \times n = 45 \quad \dots(2)$$

Solving, we get  $n = 15, m = 3$

3.(2) When Jockey is not connected  $I = \frac{E}{13r} \quad \dots(1)$

Resistance per unit length

$$\lambda = \frac{12r}{300} \Omega/cm$$

$$\therefore R_{AC} = \lambda l = \frac{12r}{300} \times 275$$


$$\therefore R_{AC} = 11r$$

Let potential at C is zero.


$$\text{At A : } \frac{x-0}{11r} + \frac{x-\frac{E}{2}-0}{2r} + \frac{(x-E-0)}{2r} = 0$$

$$\Rightarrow x = \frac{11E}{16}$$
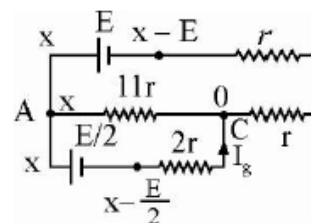
$$\therefore I_g = \frac{x-\frac{E}{2}}{2r} = \frac{\left(\frac{11E}{16}\right) - \frac{E}{2}}{2r} = \frac{3E}{32r}$$



4.(1) The circuit is

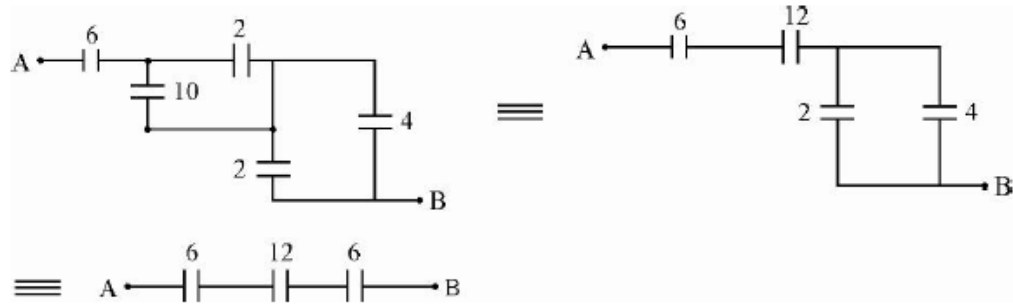

$$\therefore \frac{1}{C} = \frac{1}{6} + \frac{1}{12} + \frac{1}{6}$$


$$\Rightarrow \frac{1}{C} = \frac{5}{12}$$

$$\therefore C = \frac{12}{5} \mu F = 2.4 \mu F$$

5.(3) Charging of capacitor :

$$q = C_{eq} E \left[ 1 - e^{-\frac{t}{\tau}} \right]$$

Where,  $\tau = RC_{eq}$

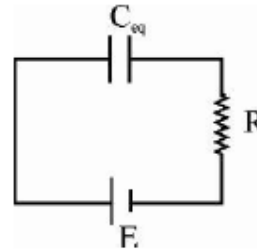

$$\therefore q = C_{eq} E \left[ 1 - e^{-\frac{t}{RC_{eq}}} \right]$$

6.(1) Switch (1) : Final charge in charging =  $C_1 V$

$$= 1 \mu F \times 60 \text{ Volt} = 60 \mu C$$

$$\text{Switch (2)} : C_{23} = \frac{C_2 C_3}{C_2 + C_3} = \frac{3 \times 6}{3 + 6} \mu F = 2 \mu F$$

$$\begin{array}{c} +60 \mu C \\ -60 \mu C \end{array} \frac{\begin{array}{c} 0 \mu C \\ 0 \mu C \end{array}}{C_1} \frac{\begin{array}{c} 0 \mu C \\ 0 \mu C \end{array}}{C_{23}} \xrightarrow{\text{Final}} \frac{\begin{array}{c} +q_1 \\ -q_1 \end{array}}{1 \mu F} \frac{\begin{array}{c} +q_2 \\ -q_2 \end{array}}{2 \mu F}$$

Charge is conserved  $\therefore q_1 + q_2 = 60 \mu C$

$V =$  common potential


$$\therefore V = \frac{q_1}{1} = \frac{q_2}{2} = \frac{q_1 + q_2}{1 + 2} = \frac{60}{3}$$

$$\therefore q_2 = 40 \mu C$$

7.(3) Final charge on capacitor =  $CV = 0.2\mu F \times 10\text{ volt} = 2\mu C$

LC Oscillation :

Initial charge =  $Q_0 = 2\mu C$

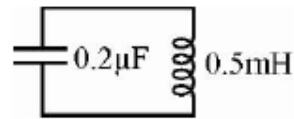

$$Q = Q_0 \cos \omega t, \text{ where } \omega = \frac{1}{\sqrt{LC}}$$

$$V = \frac{Q}{C} = \frac{Q_0}{C} \cos \omega t \Rightarrow 5 = 10 \cos \omega t$$

$\therefore \omega t = 60^\circ$

$\therefore$  Current =  $I = -\frac{dQ}{dt} = Q_0 \omega \sin \omega t$

$$\Rightarrow I = \frac{Q_0}{\sqrt{LC}} \sin 60^\circ \Rightarrow I = \frac{2 \times 10^{-6}}{\sqrt{0.5 \times 10^{-3} \times 0.2 \times 10^{-6}}} \times \frac{\sqrt{3}}{2} A$$

$\therefore I = 0.17 A$

8.(4) Figure of merit =  $\frac{I}{\theta} = 60\mu A$

$\Rightarrow I = 9 \times 60\mu A$

$\therefore I = 540\mu A$


Also,  $I = \frac{E}{R+G}$  ... (1)

$\Rightarrow 540 \times 10^{-6} = \frac{6}{11000 + G}$

$\therefore G = 111\Omega$  ... (2)

Again,  $\frac{I}{2} = \frac{E}{R + \frac{GS}{G+S}} \cdot \frac{S}{G+S}$

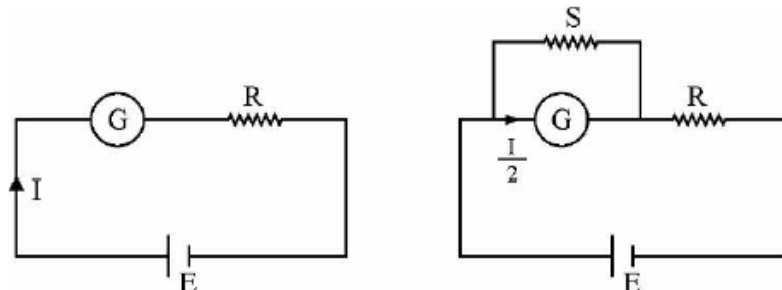$\therefore I = \frac{2SE}{RG + RS + GS}$  ... (3)



---

Equate (1) & (3),

$$\Rightarrow \frac{E}{R+G} = \frac{2SE}{RG+RS+GS} \Rightarrow RG+RS+GS = 2RS+2GS$$

$$\Rightarrow RG = RS + GS \Rightarrow \boxed{S = \frac{RG}{R+G}}$$

$$\Rightarrow S = \frac{11000 \times 111}{11111} \Omega$$

$$\therefore S = 110 \Omega$$

9.(2) Average power =  $\langle p \rangle = \frac{1}{2} \varepsilon_0 i_0 \cos \phi$

Here,  $\varepsilon_0 = 100$ ,  $i_0 = 20$ ,  $\phi = -\frac{\pi}{4}$

$$\therefore \langle p \rangle = \frac{1}{2} \times 100 \times 20 \times \cos \frac{-\pi}{4}$$

$$\langle p \rangle = \frac{1000}{\sqrt{2}}$$

$$|\text{Wattless current}| = I_{rms} \sin |\phi| = \frac{20}{\sqrt{2}} \sin \frac{\pi}{4} = \frac{20}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}}$$

$$\therefore |\text{Wattless current}| = 10.$$

10.(2) Efficiency =  $\eta = \frac{\text{output power}}{\text{Input power}}$

$$\eta = \frac{\varepsilon_s I_s}{\varepsilon_p I_p}$$

$$\Rightarrow I_s = \frac{\eta I_p \varepsilon_p}{\varepsilon_s} \Rightarrow I_s = \frac{0.9 \times 5 \times 2300}{230} A \quad \therefore I_s = 45 A$$

11.(3) Magnetic flux,  $\phi = n \vec{B} \cdot \vec{A}$

$$\phi = nBA \cos \omega t$$

$$\therefore |\text{Induced emf}| = |\varepsilon| = \left| \frac{d\phi}{dt} \right| \Rightarrow |\varepsilon| = nBA \omega |\sin \omega t|$$

$$\therefore |\varepsilon|_{\max} = nBA \omega$$

---


12.(3) By symmetry, the magnetic field at the centre P is zero.

13.(3) The centre will be at 'C' as shown:

Coordinates of the centre are  $(r \cos 60^\circ, -r \sin 60^\circ)$

Where  $r = \text{radius of circle} = \frac{mv}{Bq} = \frac{1 \times 1}{1 \times 1} = 1$

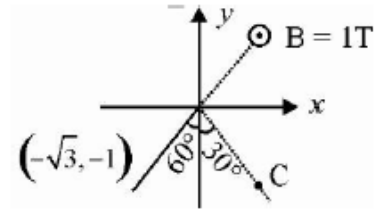i.e.,  $\left(\frac{1}{2}, -\frac{\sqrt{3}}{2}\right)$



14.(2) Magnetic field at the centre of loop due to straight wire is  $B_0 = \frac{\mu_0 I}{2\pi r} = \frac{\mu_0}{2\pi}$  tesla

Magnetic moment of the loop =  $M = NIA = 100 \times 2 \times \pi \times 4 \times 10^{-4} \text{ A} \cdot \text{m}^2$

$$\therefore M = 8\pi \times 10^{-2} \text{ A} \cdot \text{m}^2$$

$$\therefore \text{Torque acting on the loop} = |\tau| = |\vec{M} \times \vec{B}_0| = MB_0 \sin 90^\circ = MB_0 = \frac{\mu_0}{25}$$

15.(1) To demagnetise completely :  $H = 100 \text{ A/m} = nI$

$$\therefore I = \frac{H}{n} = \frac{100}{1000} \times 10^{-2} \text{ A} \Rightarrow I = 1 \times 10^{-3} \text{ A}$$

$$\therefore I = 1 \text{ mA}$$

16.(4) Assume a solid sphere without cavity.

Potential at A due to this solid sphere

$$\Rightarrow V_A' = \frac{3}{2} \cdot \frac{1}{4\pi\epsilon_0} \cdot \frac{\left(\frac{4}{3}\pi R^3 \rho\right)}{R} = \frac{\rho R^2}{2\epsilon_0}$$

Now consider the cavity filled with negative charge

$$V_A'' = \frac{1}{4\pi\epsilon_0} \cdot \frac{\frac{4}{3}\pi \left(\frac{R}{2}\right)^3 (-\rho)}{\frac{R}{2}} = \frac{-\rho R^2}{12\epsilon_0}$$

Now net value for the solid sphere with the cavity can be given by superposition of the above two cases.

$$\text{Hence, } V_A = V_A' + V_A'' = \frac{\rho R^2}{\epsilon_0} \left(\frac{1}{2} - \frac{1}{12}\right) = \frac{5\rho R^2}{12\epsilon_0}$$


17.(1) The bowl exerts a normal force N on each ball, directed along the radial line or at  $60^\circ$  above the horizontal.

Consider the free-body diagram of the ball on the left with the electric force  $F_e$  applied.

$$\sum F_y = N \sin 60^\circ - mg = 0, \Rightarrow N = mg / \sin 60^\circ$$

$$\sum F_x = -F_e + N \cos 60^\circ = 0, \Rightarrow \frac{Kq^2}{R^2} = N \cos 60^\circ = \frac{mg}{\tan 60^\circ} = \frac{mg}{\sqrt{3}}$$

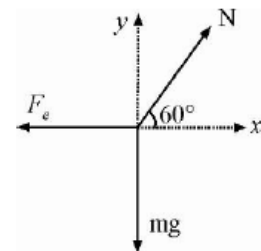
$$\text{Thus, } q = R \left( \frac{mg}{K\sqrt{3}} \right)^{1/2}$$



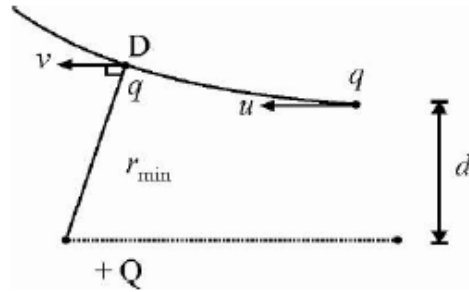- 18.(3) The path of the particle will be as shown in the figure. At the point of minimum distance (D) the velocity of the particle will be  $\perp$  to its position vector w.r.t to +Q.

Now by conservation of energy:

$$\frac{1}{2}mu^2 + 0 = \frac{1}{2}mv^2 + \frac{KQq}{r_{\min}} \quad \dots(1)$$



$\therefore$  Torque on q about Q is zero hence angular momentum about Q will be conserved  
 $\Rightarrow mvr_{\min} = mud \quad \dots(2)$

By (2) in (1)  $\Rightarrow \frac{1}{2}mu^2 = \frac{1}{2}m\left(\frac{ud}{r_{\min}}\right)^2 + \frac{KQq}{r_{\min}}$

$$\Rightarrow \frac{1}{2}mu^2\left(1 - \frac{d^2}{r_{\min}^2}\right) = \frac{mu^2d}{r_{\min}} \quad \{\because KQq = mu^2d(\text{given})\}$$

$$\Rightarrow r_{\min}^2 - 2r_{\min}d - d^2 = 0 \quad \Rightarrow r_{\min} = \frac{2d \pm \sqrt{4d^2 + 4d^2}}{2} = d(1 \pm \sqrt{2})$$

$\therefore$  Distance cannot be negative

$$\therefore r_{\min} = d(1 + \sqrt{2})$$

19.(1) Here,  $E_x = E_0 \cos 37^\circ + E_0 \cos 53^\circ = \frac{4}{5}E_0 + \frac{3}{5}E_0 = \frac{7}{5}E_0$


and  $E_y = E_0 + E_0 \sin 53^\circ - E_0 \sin 37^\circ = E_0 + \frac{4}{5}E_0 - \frac{3}{5}E_0 = E_0 + \frac{1}{5}E_0 = \frac{6F_0}{5}$

$$\therefore E_0' = \sqrt{E_x^2 + E_y^2} = \sqrt{\frac{49}{25} + \frac{36}{25}}E_0 = \sqrt{\frac{85}{25}}E_0 = \frac{\sqrt{85}}{5}E_0$$

Here,  $\tan \phi = \frac{E_y}{E_x} = \frac{\frac{6}{5}E_0}{\frac{7}{5}E_0} = \frac{6}{7}$

$$\therefore \phi = \tan^{-1}\left(\frac{6}{7}\right)$$

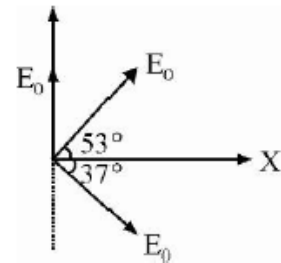Thus,  $E = E_0' \sin(\omega t + \phi) = \frac{\sqrt{85}}{5}E_0 \sin\left[\omega t + \tan^{-1}\left(\frac{6}{7}\right)\right]$




20.(1) The path difference at point P is

$$= 2l + SP + \frac{\lambda}{2} - SP$$

$$= 2l + \frac{\lambda}{2} = m\lambda$$

or  $2l = m\lambda - \frac{\lambda}{2}$

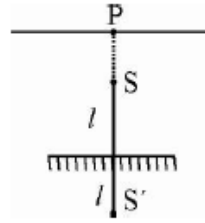$\therefore l = \frac{m\lambda}{2} - \frac{\lambda}{4}$  ... (i)



When the mirror is shifted downward at distance,  $l_0$

$$\Delta x' = 2(l + l_0) + \frac{\lambda}{2} = \left(m + \frac{1}{2}\right)\lambda$$

or  $l + l_0 = \left(m + \frac{1}{2}\right)\frac{\lambda}{2} - \frac{\lambda}{4}$

or  $m\frac{\lambda}{2} - \frac{\lambda}{4} + l_0 = m\frac{\lambda}{2} + \frac{\lambda}{4} - \frac{\lambda}{4}$

or  $l_0 = \frac{\lambda}{4} = \frac{600}{4} = 150nm$

21.(3) At path difference  $\frac{\lambda}{6}$ , phase difference is  $\frac{\pi}{3}$ .

$$I = I_0 + I_0 + 2I_0 \cos \frac{\pi}{3} = 3I_0$$

$$I_{\max} = 4I_0$$

So the required ratio is  $\frac{3I_0}{4I_0} = 0.75$

22.(3) For second minima,  $\sin \theta = \frac{2\lambda}{a}$

$$\Rightarrow \sin \theta = \frac{2 \times 550 \times 10^{-9}}{22 \times 10^{-7}} \Rightarrow \sin \theta = \frac{1}{2} \Rightarrow \theta = 30^\circ = \frac{\pi}{6}$$

23.(3) Let Angle between the direction of polarization and x-axis is  $\alpha$ .


Let  $\beta$  is angle between polarization and pass axis.

$$\beta = \alpha - \theta, \text{ if } 180^\circ < \theta < 270^\circ$$

Also,  $\beta_1 = -\beta_2$  at  $\theta_1 = 188^\circ$  and  $\theta_2 = 218^\circ$

$$\Rightarrow \alpha - 188^\circ = -(\alpha - 218^\circ)$$

$$\therefore \alpha = 203^\circ$$

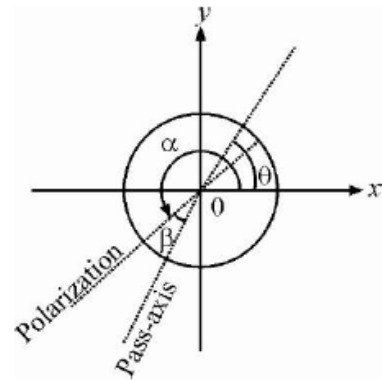

24.(2)  $\therefore -\frac{1}{20} = (1.5 - 1) \left( -\frac{1}{R} - \frac{1}{R} \right)$

or  $-\frac{1}{20} = -\frac{1}{R}$

$$\therefore R = 20 \text{ cm}$$

$$\therefore \text{The power of the silvered lens is } P = 2P_l + P_m = -\frac{2}{20} - \frac{1}{10} = -\frac{2}{10} = -\frac{1}{5}$$

The focal length of equivalent mirror is,

$$F = -\frac{1}{P} = 5 \text{ cm}$$

$$\therefore \frac{1}{v} + \frac{1}{u} = \frac{1}{f}$$

or  $\frac{1}{v} - \frac{1}{40} = \frac{1}{5}$

$$\therefore v = \frac{40}{9} \text{ cm}$$

25.(2)  $x = x_0 + A \sin \omega t$

$$\therefore x = 10 + 2 \sin \omega t$$

$$\therefore u = -(10 + 2 \sin \omega t)$$

(A) periodic motion

(C) Right amplitude  $A_2 = \frac{40}{3} - 10 = \frac{10}{3} \text{ cm}$ ,

Left amplitude  $A_1 = 10 - \frac{60}{7} = \frac{10}{7} \text{ cm}$

(D)  $\therefore v = \frac{fu}{u-f}, f = -5 \text{ cm}$

Image position :

When  $x = 8 \text{ cm}$ ,

$$v_1 = \frac{(-5) \times (-8)}{-8+5} \text{ cm} = -\frac{40}{3} \text{ cm}$$



---

When  $x = 12\text{ cm}$ ,

$$v_2 = \frac{(-5) \times (-12)}{-12 + 5} \text{ cm} = -\frac{60}{7} \text{ cm}$$

$$\therefore \text{Distance between turning points} = |v_1| - |v_2| = \frac{40}{3} - \frac{60}{7} = \frac{100}{21} \text{ cm.}$$

$\therefore$  Correct options are A, C, D

26.(2) Total deviation  $\delta = i - r + 180^\circ - 2r + 180^\circ - 2r + i - r$

$$\delta = 360^\circ + 2i - 6r$$

For minimum  $\delta$ ,  $\frac{d\delta}{di} = 0$

$$\Rightarrow 2 - 6 \frac{dr}{di} = 0 \quad \Rightarrow \quad \frac{dr}{di} = \frac{1}{3} \quad \dots(1)$$

Snell's law

$$1 \sin i = \mu \sin r \quad \Rightarrow \quad \cos i \cdot di = \mu \cos r \cdot dr \quad \dots(2)$$

$$\therefore \text{By (1) \& (2)., } \cos i = \frac{\mu \cos r}{3}$$

$$\Rightarrow \cos i = \frac{\mu}{3} \sqrt{1 - \sin^2 r} = \frac{\mu}{3} \sqrt{1 - \frac{\sin^2 i}{\mu^2}}$$

$$\Rightarrow \sqrt{\mu^2 - \sin^2 i} = 3 \cos i \quad \Rightarrow \quad \mu^2 - 1 = 8 \cos^2 i$$

$$\therefore \cos i = \sqrt{\frac{\mu^2 - 1}{8}}$$

27.(3) Higher frequency causes photoemission of electron with largest kinetic energy

$$= f = \frac{\omega}{2\pi} = \frac{8 \times 10^{15}}{2\pi} \text{ s}^{-1}$$

Maximum kinetic energy of photoelectrons is:

$$K_{\max} = hf - \phi_0 = \frac{4.14 \times 10^{-15} \times 8 \times 10^{15}}{2\pi} - 2.0 = 5.27 - 2.0 = 3.27 \text{ eV}$$

28.(4) After  $t$  seconds,  $\frac{N_A}{N_B} = \frac{N_0 e^{-10\lambda t}}{N_0 e^{-\lambda t}} = \frac{e^{-10\lambda \times 1/9\lambda}}{e^{-\lambda \times 1/9\lambda}} = \frac{e^{-\frac{10}{9}}}{e^{-\frac{1}{9}}} = e^{\left(\frac{10}{9} - \frac{1}{9}\right)} = e^{-9/9} = e^{-1}$

---

---

29.(4) First we find the location of COM

$$Mx = m(r - x)$$

$$x = \left( \frac{m}{M + m} \right) r \quad \dots(i)$$

Centripetal force an electron is due to electrostatic attraction.

$$\text{So, } m(r - x)\omega^2 = K \frac{Ze^2}{r^2} \Rightarrow m \left( r - \frac{mr}{M + m} \right) \omega^2 = \frac{KZe^2}{r^2}$$

$$\Rightarrow \left( \frac{m}{M + m} \right) Mr \omega^2 = \frac{KZe^2}{r^2} \Rightarrow \left( \frac{Mm}{M + m} \right) r^3 \omega^2 = KZe^2 \quad \dots(ii)$$

Where,  $\frac{Mm}{M + m} = \mu =$  reduced mass of system

$$\text{Now, moment of inertia of system} = I = Mx^2 + m(r - x)^2$$

Now, we substitute for  $x$  from Equation (i) in above expression, we get

$$I = M \left( \frac{m}{M + m} \right)^2 r^2 + m \left( r - \frac{mr}{M + m} \right)^2 = \frac{Mm^2 r^2 + mM^2 r^2}{(M + m)^2} = \left( \frac{Mm}{M + m} \right) r^2 = \mu r^2$$

$$\therefore \text{Angular momentum} = I\omega = \left( \frac{Mm}{M + m} \right) r^2 \omega.$$

30.(1) Current gain =  $\beta = \frac{\Delta I_C}{\Delta I_B}$  ; Voltage gain =  $\beta \cdot \frac{R_L}{R_{BE}}$

$$\text{Power gain} = \beta^2 \cdot \frac{R_L}{R_{BE}}$$

◆◆◆

---